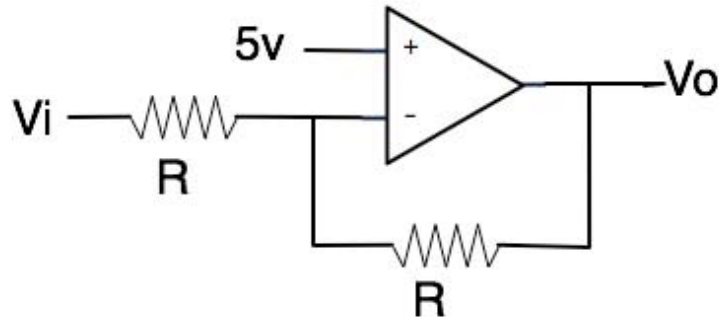


Problem Wk.8.3.3: Op Amp practice

Part 1: Op Amps

1. Consider the following circuit:



Note that both resistors have the same value.


If $V_i = 4$, then $V_o =$

If $V_i = 8$ then $V_o =$

If $V_i = 10$ then $V_o =$

Part 2: Op Amps

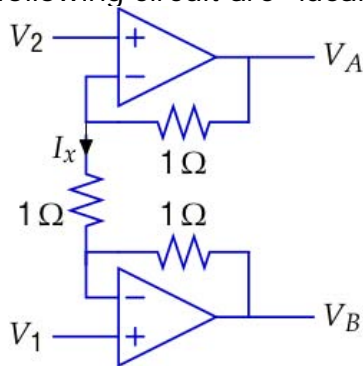1. Assume the op-amps in the following circuit are "ideal."



Determine the current I_x when $V_1 = 1$ Volts and $V_2 = 2$ Volts.

Amps (as decimal number)

Determine the voltage V_A when $V_1 = 1$ Volts and $V_2 = 2$ Volts.

Volts (as decimal number)

Determine a general expression for V_A in terms of V_1 and V_2 . Enter the coefficients as decimal numbers:

$$V_A = \boxed{} * V_1 + \boxed{} * V_2$$

MIT OpenCourseWare
<http://ocw.mit.edu>

6.01SC Introduction to Electrical Engineering and Computer Science
Spring 2011

For information about citing these materials or our Terms of Use, visit: <http://ocw.mit.edu/terms>.